


Lab 10 : Digital CPU Foundations (Gates → Subcircuits → PC & Memory)

Objectives:

- Create and simulate the minimal 4-bit ISA
- **CPU goal:**
 - Instruction: 8 bits
 - Data width: 4 bits
 - Registers: 8 register - R0–R7 (four 4-bit regs)
 - Data RAM: 8 locations (3-bit address), each 4-bit
 - Program ROM: 16 locations (4 bits), each 9-bit instruction
 - Instruction: 9-bit
 - **LDR** – Load from register (Opcode 000): $Rd = Rs$ Format: 000 | $Rd[2:0]$ | $Rs[2:0]$
 - **LDM** – Load from memory (Opcode 001): $Rd = [Addr]$ Format: 001 | $Rd[2:0]$ | $Src[2:0]$
 - **LDI** – Load Immediate (Opcode 010): $Rd = \#Immediate$ Format: 010 | $Rd[2:0]$ | $\#Immediate$
 - **STR** – Store to memory (Opcode 011): $[Addr] = Rs$ Format: 011 | $Rs[2:0]$ | $Dest[2:0]$
 - **ADD** – Add register (opcode 100): $Rd = Rd + Rs$ Format: 100 | $Rd[2:0]$ | $Rs[2:0]$
 - **BZ** – Branch if zero (Opcode 101): If Zero, branch Format: 101 | 00 | $Addr[3:0]$
 - **Legend:**
 - **Rd**: Destination register (3 bits).
 - **Rs**: Source register (3 bits).
 - **Src**: data at source address (3 bits).
 - **Dest**: data at destination address (3 bits).
 - **Immediate** : Constant (3 bits).
 - **Addr**: address in ROM (4 bits)

Lab 10.1 : Install and launch

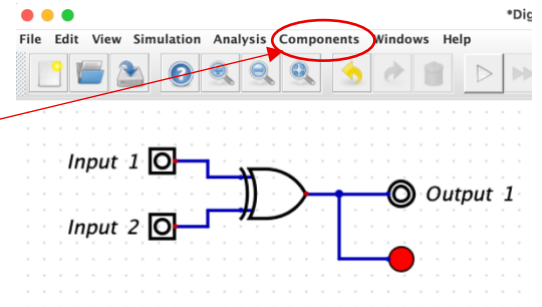
1. Download the latest **Digital.jar** file from the official GitHub repository:
<https://github.com/hneemann/Digital/releases>
2. Ensure you have Java installed on your system (Mac, Windows, or Linux).
3. Run program by launch Digital.jar. If it doesn't start, run: `java -jar Digital.jar`
4. Create a XOR Gate with two inputs and one output by
 - 4.1. Add 2 inputs : Components -> IO -> **Input**.
 - 4.2. Add output: Components -> IO -> **Output**.
 - 4.3. Label both input and putput by right click on component and label it.
 - 4.4. Add XOR-Gate : Components -> Logic -> **XOR**.
 - 4.5. Wire inputs , output to the gate.
 - 4.6. Simulate by click on the **play button** located in the toolbar.
 - 4.7. Try to change inputs and notices output.
5. To further process the circuit, the simulation must first be stopped with the **stop button** in the tool bar
6. At menu bar "Analysis", try Analysis and Synthesis.



TA Cecking: Show the TA simulated XOR circuit and its truth table. _____

Lab 10.2 : Hierarchical Design: Adder / ALU

 1. Make new circuit for half adder as: $sum = A \oplus B$ (A XOR B) , $Carry = A \cdot B$ (A AND B).
2. Save as "**halfAdder.dig**".
3. Create new empty file and save as "**fullAdder.dig**".



TA Checking: Demonstrate the complete latching mechanism of your ALU's Zero Flag. _____

1. Set for Zero: Input values that result in zero (e.g., A=5, B=11 for 5 + (-5) in 4-bit two's complement). Show that the combinational logic (the NOR gate output) is 1.
 2. Latch the '1': With FlagWrite set to 1, advance the Clock by one tick. Show that the final Zero_Flag output is now latched and holding the value 1.
 3. Hold the '1': Change the inputs to a non-zero result (e.g., A=2, B=3). Show that the NOR gate output is now 0.
 4. Demonstrate Unlatch Condition: With FlagWrite set to 0, advance the Clock. Show that the Zero_Flag output *remains* 1, proving that the register is correctly holding the previous value and ignoring the new input.
 5. Latch the '0': Set FlagWrite back to 1 and advance the Clock. Show that the Zero_Flag output now updates to 0.
-

Lab 10.4 : Register File

1. Create the Register File Circuit:
 - 1.1. Create a new file and save it as "**registerFile.dig**".
 - 1.2. Add a Register File component from Components -> Memory - RAM -> Register File.
 - 1.3. Configure Properties: Right-click the component and set:
 - 1.3.1. Data Bits: 4
 - 1.3.2. Address Bits: 3 (3 bits can address 8 unique registers, R0 to R7).
 - 1.4. Add and connect input: : 4-bit to **Din** (data in), 1-bit to **we** (write enable), 3-bit **Rw** (register to be written), 1-bit to **C** (clock), 3-bit to **Ra** and **Rb**.
 - 1.5. Add and connect output: 4-bit to Da and 4-bit to Db
 - 1.6. Click "Play" for simulation. Right click to see the data.

TA Checking:

1. **Write to R2:** _____
 - 1.1. Set we (Write Enable) to **1**.
 - 1.2. Set Rw (Write Address) to **10** (binary for 2).
 - 1.3. Set Din (Data In) to **0111** (binary for 7).
 - 1.4. Advance the Clock one tick. The value 7 is now stored in R2.
 - 1.5. Right click on register file to see data.
 - 1.6. **Disable Write:** Set we back to **0**.
 2. **Read from R2 on Port A:** Set Ra (Read Address A) to **10**. Show that the Da output is now **0111**. _____
 3. **Read from R2 on Port B:** Set Rb (Read Address B) to **10**. Show that the Db output is also **0111**. _____
 4. **Verify Independence:** Write a different value (e.g., 5) to a different register (e.g., R1, address 01) and show you can read it back without affecting the value in R2. _____
-

Lab 10.5: Program Counter and Memory (ROM and RAM)

Part A: Program Counter (PC)

1. Create the PC Circuit:
 1. Create a new file, "**programCounter.dig**".
 2. Add a Counter with preset from Components -> Memory -> Counter with preset.
 3. Configure Properties: Set Data Bits to 4.
 4. Add Output: **out**: 4-bit Output. This is the current address sent to the Program ROM.
 5. Connect the counter's **en** (enable) pin to a **Supply voltage** (Components -> Wires -> Supply voltage) to ensure it's always enabled to count.
 6. Connect the **dir** pin to a **Ground component** (Components -> Wires -> Ground).
 7. Add input : 1-bit to **C**, 4-bit to **in**, 1-bit to **ld**, 1-bit to **clr**.
 8. Ass output: 3-bit to **out**.
 9. Save the circuit.

TA Checking:

1. Output count form 0 to 7 and back to 0 on every **clock** tick. _____
2. Set data **in** and **ld** = 1 and clock tick, output the data in. _____
3. Clear to 0 when clr is 1 and clock tick. _____

Part B: Program ROM

1. Create the ROM Circuit:
 1. Create a new file, "**programROM.dig**".
 2. Add a ROM component from Components -> Memory -> ROM.
 3. Configure Properties:
 - Address Bits: 3
 - Data Bits: 8
 4. Connect the 3-bit address Input to the **A** pin of the ROM.
 5. Connect the 8-bit instruction Output to the **D** pin of the ROM.
 6. Connect the **sel** (select) pin to a Supply voltage component (Components -> Wires -> Supply voltage).
 7. Load Program: Right-click the ROM component and select "Edit Content". Enter the 8-bit instructions.
 8. Save the circuit.

TA Checking: Load instruction into ROM, set address to see the correct output. _____

Part C: Data RAM

1. Create the RAM Circuit:
 1. Create a new file, "**dataRAM.dig**".
 2. Add a RAM, separated Ports component from Components -> Memory - RAM -> RAM, separated Ports.
 3. Configure Properties:
 - Address Bits: 3
 - Data Bits: 4
 4. Inputs: Addr (Address): 3-bit to **A**, **Din** (Data In): 4-bit, **str** (Store): 1-bit, **ld** (Load): 1-bit Input. **C** (Clock): 1-bit.
Output: Dout (Data Out): 4-bit Output.
 5. Click "Play" to simulate the RAM. Right click to see the data

TA checking: Store and read data from RAM : _____

1. To store data: set address to Addr, set data **Din**, **MemWrite** = High, **clock** tick
2. To load data: set address to Addr, **MemRead** = High, **clock** tick

Lab 10.6: Multiplexer

A Multiplexer selects exactly one of N data inputs and forwards it to the output based on a selector (sel).

1. Create new file. Add multiplexer on canvas (Components -> Plexers -> Multiplexer).
2. Set data bits = 4, Selector bits = 2. This will create multiplexer with 4 4-bit input (in_0, in_1, in_2, in_3) and 2-bit selector 00 output from **in_0**, 01 output from **in_1**, 10 output from **n_2** and 11 output from **n_4**.
3. Add 4-bit input to **in_0**, **in_1**, **in_2**, **in_3**.
4. Add 4-bit output to **out**.
5. Set difference data for each input, set selector and observ the result.

TA checking: _____

LAB Submission

https://docs.google.com/forms/d/e/1FAIpQLSdFhcWXLzpc5v1fWzFxQ9mqXijq-1aHaBRmQkgNIX_Dh2eLJQ/viewform?usp=header